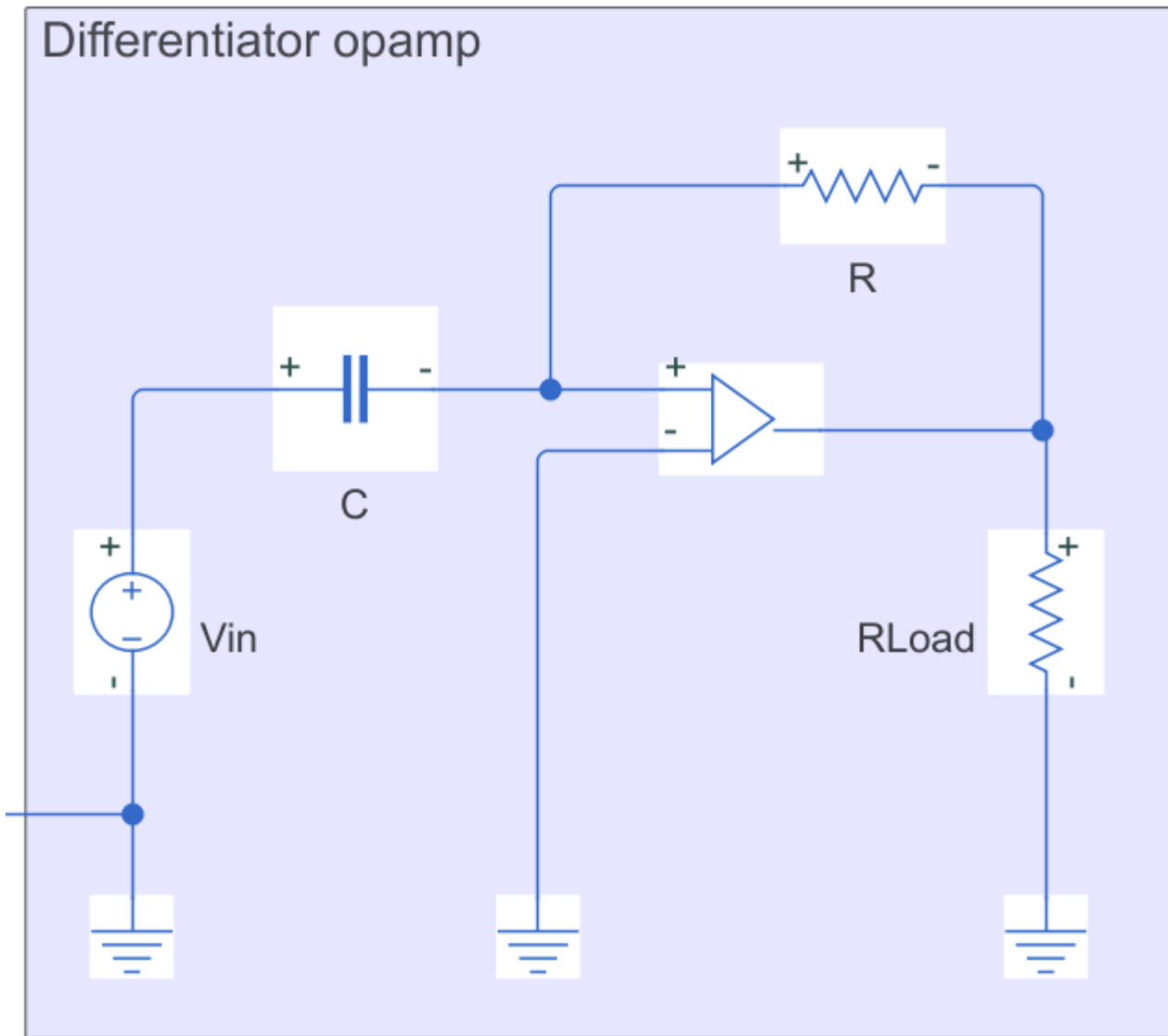


Differentiators and integrators derivation



Since there are zero current and voltage through and across the opamp terminals,

$KVL_1 :$

$$V_{in} = V_c$$

and

$KVL_2 :$

$$KVL_2 : -V_{in} + V_c + R \times i + V_o = 0$$

From a current and voltage characteristic behavior of a capacitor, we've got


$$i = C \frac{dV_c}{dt}$$

therefore

$$V_o = -RC \frac{dV_c}{dt} \text{ and, since } V_{in} = V_c,$$

$$V_o = -RC \frac{dV_{in}}{dt}$$

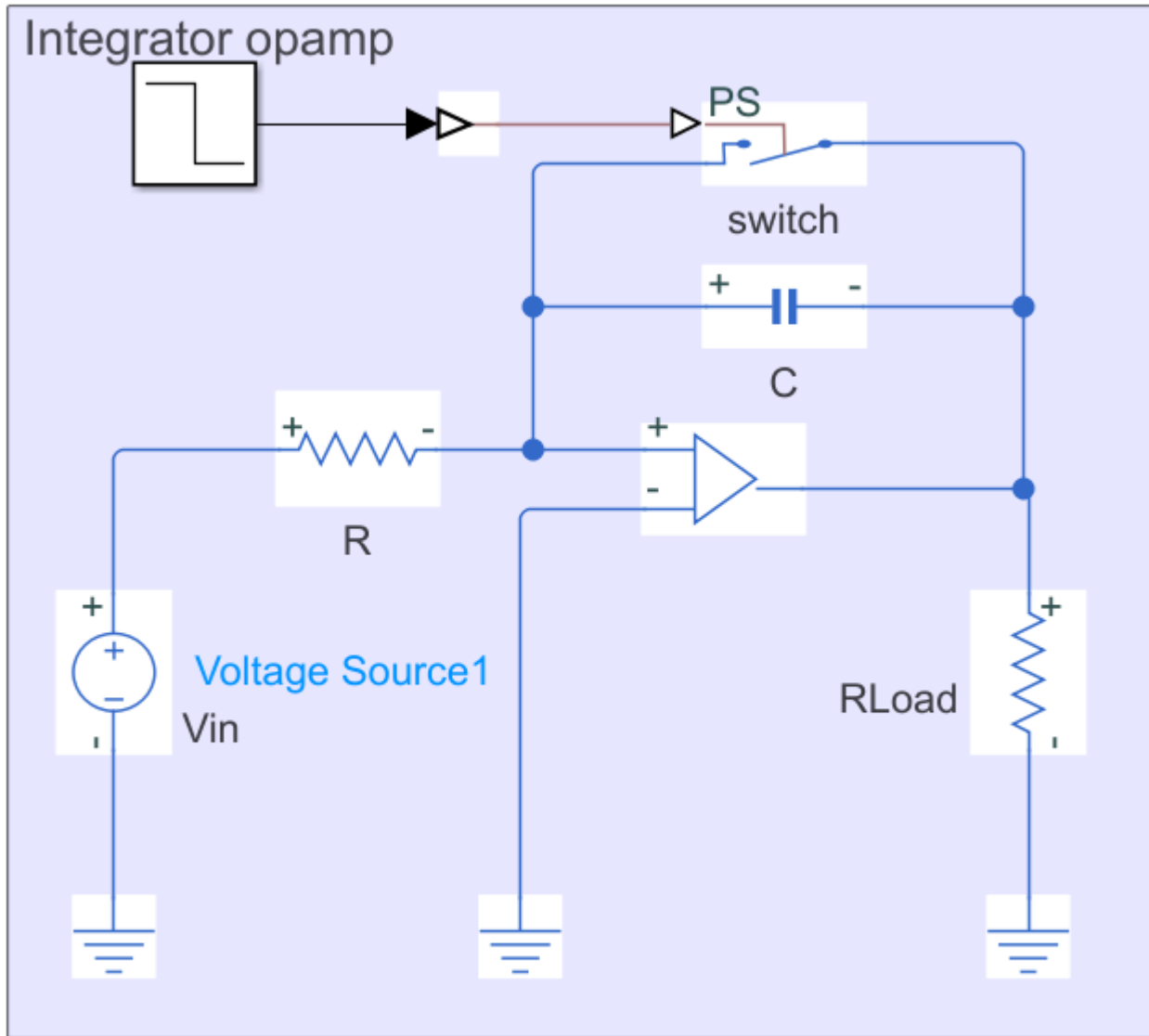The $-RC$ constant is the gain of this circuit, our design goal is to chose a value of RC that's meet some requirement.



The analysis is the same as before, except that we have a switch that controls how the current will flow through the circuit

For $t < 0$:

KVL_1 :

$$V_{in} = iR$$

and

$KVL_2 : -V_{in} + iR + V_o = 0$, therefore $V_o = 0$

For $t > 0$:

$KVL_2 :$

$-V_{in} + iR + V_c + V_o = 0$ and again using the current and voltage characteristic equation, $i = C \frac{dV_c}{dt}$, but using

integral calculus to get the voltage across the capacitor $V_c = \frac{1}{C} \int_0^t i dt$, we've got

$$V_o = -\frac{1}{C} \int_0^t i dt$$

or using the relationship $i = \frac{V_{in}}{R}$

$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt$$

The $\frac{-1}{RC}$ constant is the gain of this circuit, our design goal is to chose a value of RC that's meet some requirement.