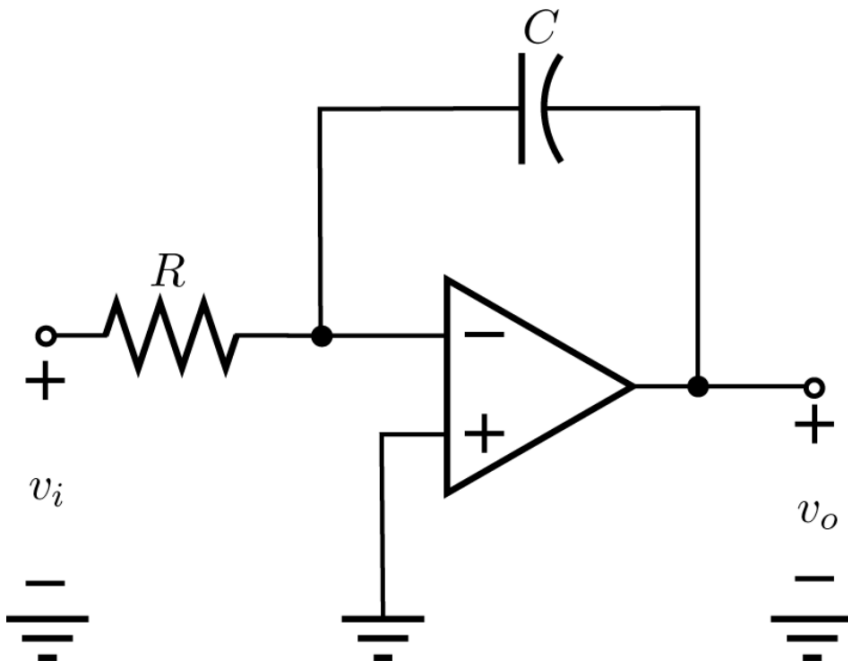


## Problem 2.4.1



For the circuit above,  $R = 4\text{M}\Omega$  and  $C = 0.75\mu\text{F}$ .  $v_i(t) = -t^2\text{V}$  for  $s \leq t \leq 5\text{s}$ . What is the value of  $v_o$  at time  $t = 5\text{s}$ , if  $v_o(0) = 0$ ? You can assume the operational amplifier behaves as an ideal op amp with power supplies of  $+15\text{V}$  and  $-15\text{V}$ .

```
syms vin(t) vo(t)
C = 0.75e-6;
R = 4e6;
ode = diff(vin, t) == -t^2; % definition of a differential equation
cond = vin(0) == 0;
% Compute analytic solution of a symbolic equation
vinSol(t) = dsolve(ode,cond);
```

vinSol(t) =

$$-\frac{t^3}{3}$$

```
% Compute analytic solution of a symbolic equation
```

```
vo(t) = (-1/(R*C))*vinSol
```

vo(t) =

$$\frac{t^3}{9}$$

vo(5)

ans =

$$\frac{125}{9}$$